

General Aptitude

Q. No. 1 – 5 Carry One Mark Each

1. Find the missing sequence in the letter series below:

A, CD, GHI,?, UVWXY

(A) LMN


(B) MNO

(C) MNOP

(D) NOPQ

Answer: (C)

Exp:

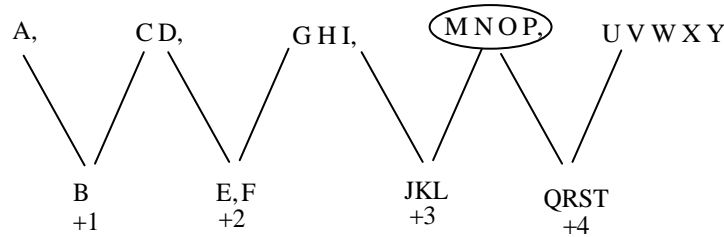

2. Choose the correct verb to fill in the blank below:

Let us _____.

(A) Introvert

(B) alternate

(C) atheist

(D) altruist

Answer: (B)

3. Choose the most appropriate word from the options given below to complete the following sentence?

If the athlete had wanted to come first in the race, he _____ several hours every day.

(A) Should practice

(B) Should have practised

(C) Practised

(D) Should be practicing

Answer: (B)

Exp: For condition regarding something which already happened, should have practiced is the correct choice.

4. Choose the most suitable one word substitute for the following expression

Connotation of a road or way

(A) Pertinacious

(B) Viaticum

(C) Clandestine

(D) Ravenous

Answer: (B)

5. If $x > y > 1$, which of the following must be true?

(i) $\ln x > \ln y$

(ii) $e^x > e^y$

(iii) $y^x > x^y$

(iv) $\cos x > \cos y$

(A) (i) and (ii)

(B) (i) and (iii)

(C) (iii) and (iv)

(D) (ii) and (iv)

Answer: (A)

Exp: For whole numbers, greater the value greater will be its log.
Same logic for power of e.

Q. No. 6 – 10 Carry Two Marks Each

6. From a circular sheet of paper of radius 30cm, a sector of 10% area is removed. If the remaining part is used to make a conical surface, then the ratio of the radius and height of the cone is _____.

Answer: 2.06

Exp: 90% of area of sheet = Cross sectional area of cone

$$\Rightarrow 0.9 \times \pi \times 30 \times 30 = \pi \times r_1 \times 30$$

$$\Rightarrow 27 \text{ cm} = r_1$$

$$\therefore \text{Height of the cone} = \sqrt{30^2 - 27^2}$$
$$= 13.08 \text{ cm}$$

$$\text{Then } r/h = 27/13.08 = 2.06$$

7. In the following question, the first and the last sentence of the passage are in order and numbered 1 and 6. The rest of the passage is split into 4 parts and numbered as 2,3,4, and 5. These 4 parts are not arranged in proper order. Read the sentences and arrange them in a logical sequence to make a passage and choose the correct sequence from the given options.

1. One Diwali, the family rises early in the morning.
2. The whole family, including the young and the old enjoy doing this,
3. Children let off fireworks later in the night with their friends.
4. At sunset, the lamps are lit and the family performs various rituals
5. Father, mother, and children visit relatives and exchange gifts and sweets.
6. Houses look so pretty with lighted lamps all around.

(A) 2, 5, 3, 4

(B) 5, 2, 4, 3

(C) 3, 5, 4, 2

(D) 4, 5, 2, 3

Answer: (B)

8. Ms. X will be in Bagdogra from 01/05/2014 to 20/05/2014 and from 22/05/2014 to 31/05/2014. On the morning of 21/05/2014, she will reach Kochi via Mumbai

Which one of the statements below is logically valid and can be inferred from the above sentences?

(A) Ms. X will be in Kochi for one day, only in May

(B) Ms. X will be in Kochi for only one day in May

(C) Ms. X will be only in Kochi for one day in May

(D) Only Ms. X will be in Kochi for one day in May.

Answer: (B)

9. $\log \tan 1^\circ + \log \tan 2^\circ + \dots + \log \tan 89^\circ$ is
- (A) 1 (B) $1/\sqrt{2}$ (C) 0 (D) -1

Answer: (C)

Exp: $\log \tan 1^\circ + \log \tan 89^\circ = \log(\tan 1^\circ \times \tan 89^\circ)$
 $= \log(\tan 1^\circ \times \cot 1^\circ)$
 $= \log 1$
 $= 0$


Using the same logic total sum is '0'.

10. Ram and Shyam shared a secret and promised to each other that it would remain between them. Ram expressed himself in one of the following ways as given in the choices below. Identify the correct way as per standard English.
- (A) It would remain between you and me.
 (B) It would remain between I and you
 (C) It would remain between you and I
 (D) It would remain with me.

Answer: (A)



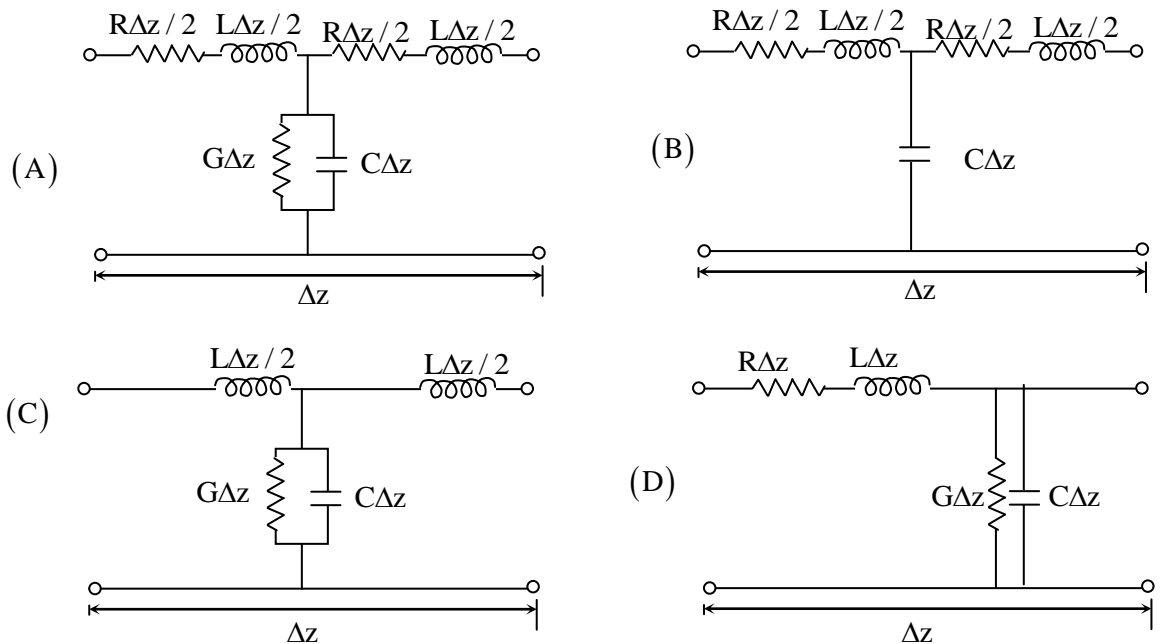1. A coaxial cable is made of two brass conductors. The spacing between the conductors is filled with Teflon ($\epsilon_r = 2.1$, $\tan \delta = 0$). Which one of the following circuits can represent the lumped element model of a small piece of this cable having length Δz ?



Answer: (B)

Exp: $V_{EB} = 0.7V$
 $I_B = 0.0383mA$
 $I_C = 1.916mA$
 $V_{EC} = 3 - I_C R_C = 3 - (1.916 \times 0.5) = 2.04V$

5. The contour on the x - y plane, where the partial derivative of $x^2 + y^2$ with respect to y is equal to the partial derivative of $6y + 4x$ with respect to x , is
 (A) $y = 2$ (B) $x = 2$
 (C) $x + y = 4$ (D) $x - y = 0$

Answer: (A)


Exp: The partial derivative of $x^2 + y^2$ with respect to y is $0 + 2y \Rightarrow 2y$.
 The partial derivative of $6y + 4x$ with respect to x is $0 + 4 = 4$.
 Given that both are equal.
 $\Rightarrow 2y = 4 \Rightarrow \boxed{y = 2}$

6. For $A = \begin{bmatrix} 1 & \tan x \\ -\tan x & 1 \end{bmatrix}$ the determinant of $A^T A^{-1}$ is
 (A) $\sec^2 x$ (B) $\cos 4x$ (C) 1 (D) 0

Answer: (C)


Exp: $|A^T A^{-1}| = |A^T| |A^{-1}| = 1$

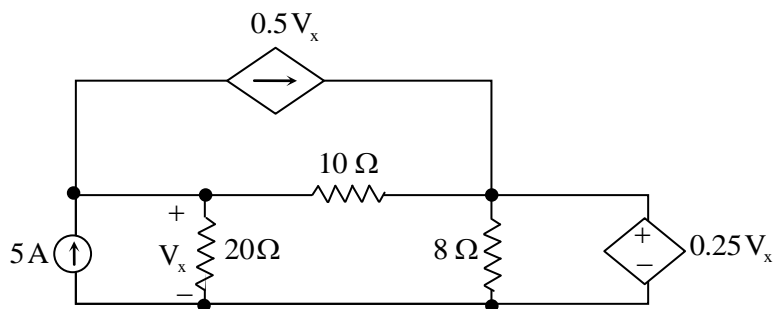7. In the circuit shown, the voltage V_x (in Volts) is_____.



Answer: 8

Exp:

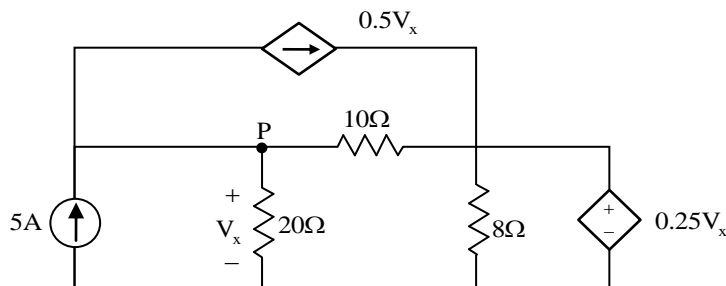

Apply KCL at point P

$$\frac{V_x}{20} + \frac{V_x - 0.25V_x}{10} + 0.5V_x = 5$$

$$V_x \left(\frac{1}{20} + \frac{0.75}{10} + 0.5 \right) = 5$$

$$V_x \left(\frac{5}{8} \right) = 5 \Rightarrow V_x = 8V$$

8. Which one of the following 8085 microprocessor programs correctly calculates the product of two 8-bit numbers stored in registers B and C?(Options)

- | | |
|---|---|
| (A) MVI A, 00 H
JNZ LOOP
CMP C
LOOP DCR B
HLT | (B) MVI, A, 00H
CMP C
LOOP DCR B
JNZ LOOP
HLT |
| (C) MVI A, 00H
LOOP ADD C
DCR B
JNZ LOOP
HLT | (D) MVI A, 00H
ADD C
JNZ LOOP
LOOP INR B
HLT |

Answer: (C)

Exp: MVI A, 00H ← Load accumulator by 00H

Loop: ADDC ← Add the content of accumulator with content of C register and store result in accumulator.

This will continue till B register reaches to 004.

DCRB
JNZ LOOP
HLT

So, repetitive addition of a number as many times will give the product of these two numbers.

9. Consider the function $g(t) = e^{-t} \sin(2\pi t) u(t)$ where $u(t)$ is the unit step function. The area under $g(t)$ is _____.

Answer: 0.155

Exp: $g(t) = e^{-t} \sin(2\pi t) \cdot u(t)$

Let $y(t) = \sin(2\pi t) \cdot u(t)$

$$\text{then } Y(s) = \frac{2\pi}{s^2 + (2\pi)^2}$$

$$g(t) = e^{-t}y(t)$$

$$\Rightarrow G(s) = Y(s+1)$$


$$G(s) = \frac{2\pi}{(s+1)^2 + (2\pi)^2}$$

$$G(s) = \int_{-\infty}^{\infty} g(t).e^{-st} dt$$

$$G(0) = \int_{-\infty}^{\infty} g(t).dt$$

$$\Rightarrow \text{Area under } g(t) = \frac{2\pi}{1+(2\pi)^2} = \frac{6.28}{40.438} = 0.155$$

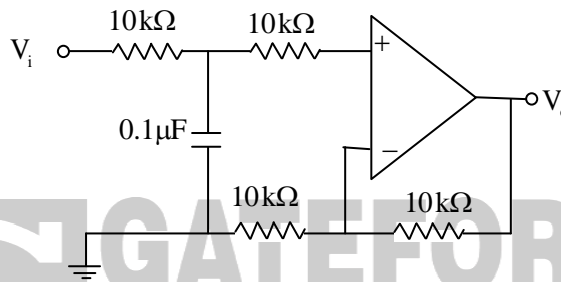10. In the circuit shown using an ideal opamp, the 3-dB cut-off frequency (in Hz) is _____.



Answer: 159.15

Exp: $f_{3dB} = \frac{1}{2\pi RC}$

$$= \frac{1}{2\pi \times 10 \times 10^3 \times 0.1 \times 10^{-6}} = 159.15\text{Hz}$$

11. The modulation scheme commonly used for transmission from GSM mobile terminals is
- (A) 4-QAM
 - (B) 16-PSK
 - (C) Walsh-Hadamard orthogonal codes
 - (D) Gaussian Minimum Shift Keying (GMSK)


Answer: (D)

12. Which one of the following processes is preferred to form the gate dielectric (SiO₂) of MOSFETs?
- (A) Sputtering
 - (B) Molecular beam epitaxy
 - (C) Wet oxidation
 - (D) Dry oxidation

Answer: (D)

Answer: 10

Exp:

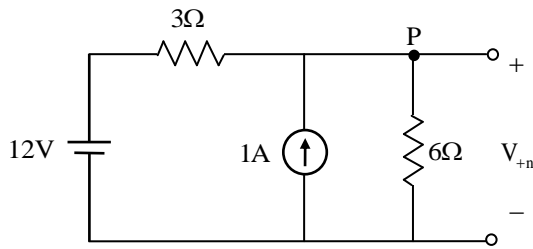

Apply nodal equation at point P


$$V_{+n} \left(\frac{1}{3} + \frac{1}{6} \right) = \frac{12}{3} + 1$$

$$\frac{V_{+n}}{2} = 5 \Rightarrow V_{+n} = 10V$$

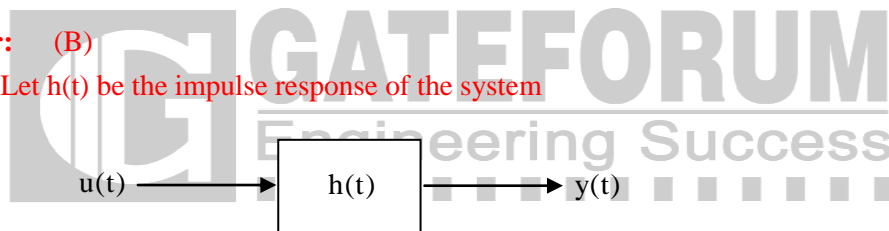19. The impulse response of an LTI system can be obtained by
- (A) differentiating the unit ramp response
 - (B) differentiating the unit step response
 - (C) integrating the unit ramp response
 - (D) integrating the unit step response

Answer: (B)

Exp: Let $h(t)$ be the impulse response of the system



$y(t)$ is unit step response of the system

$$y(t) = \int_{-\infty}^t h(\tau) d\tau$$

If we need to get $h(t)$, then we have to differentiate $y(t)$.

Thus differentiating the unit-step response gives impulse response for LTI system.

20. Consider a four point moving average filter defined by the equation $y[n] = \sum_{i=0}^3 \alpha_i [n-i]$
The condition on the filter coefficients that results in a null at zero frequency is
- (A) $\alpha_1 = \alpha_2 = 0; \alpha_0 = -\alpha_3$
 - (B) $\alpha_1 = \alpha_2 = 1; \alpha_0 = -\alpha_3$
 - (C) $\alpha_0 = \alpha_3 = 0; \alpha_1 = \alpha_2$
 - (D) $\alpha_1 = \alpha_2 = 0; \alpha_0 = \alpha_3$

Answer: (A)

Exp: Given $y[n] = \sum_{i=0}^3 \alpha_i x[n-i]$

$$\Rightarrow y[n] = \alpha_0 x[n] + \alpha_1 x[n-1] + \alpha_2 x[n-2] + \alpha_3 x[n-3]$$

Getting a null at zero frequency implies that given filter can be high pass filter but it cannot be low pass filter.

High pass filter is possible if we have negative coefficients.

Let say, $\alpha_1 = \alpha_2 = 0, \alpha_0 = -\alpha_3$

$$\Rightarrow y[n] = -\alpha_3 x[n] + \alpha_3 x[n-3]$$

$$H(z) = -\alpha_3 [1 - z^{-3}]$$

$$\Rightarrow H(e^{j\Omega}) = -\alpha_3 [1 - e^{-j3\Omega}]$$

$$= -\alpha_3 e^{-j\frac{3\Omega}{2}} \left[\frac{e^{j\frac{3\Omega}{2}} - e^{-j\frac{3\Omega}{2}}}{2j} \right] \times 2j$$

$$= -\alpha_3 2j \sin\left(\frac{3\Omega}{2}\right) e^{-j\frac{3\Omega}{2}}$$

$$= -\alpha_3 2 \sin\frac{3\Omega}{2} e^{-j\frac{3\Omega}{2}} e^{j\frac{\pi}{2}}$$

$$\Rightarrow H(e^{j\Omega}) \Big|_{\Omega=0} = 0$$

In other cases it is not possible.

21. If C is a circle of radius r with centre z_0 , in the complex z -plane and if n is a non-zero

integer, then $\oint \frac{dz}{(z-z_0)^{n+1}}$ equals

- (A) $2\pi nj$ (B) 0 (C) $\frac{nj}{2\pi}$ (D) $2\pi n$


Answer: (B)

Exp: By Cauchy's Integral formula,

$$\oint_c \frac{f(z)}{(z-z_0)^{n+1}} dz = \frac{2\pi i \cdot f^n(z_0)}{n!}$$

$$\oint_c \frac{dz}{(z-z_0)^{n+1}} = \frac{2\pi i}{n!} \times 0 = 0 \quad \left(\begin{array}{l} \because f(z) = 1 \\ f^n(z) = 0 \text{ at any } z_0 \end{array} \right)$$

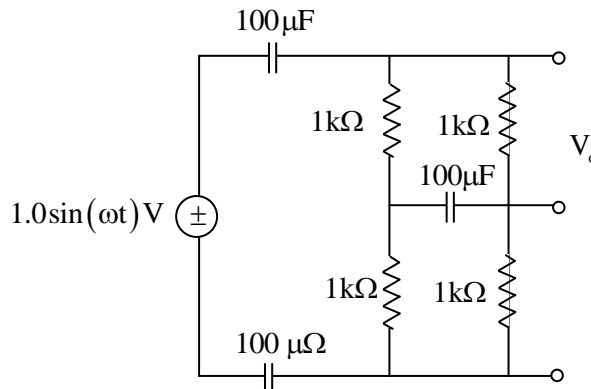22. At very high frequencies, the peak output voltage V_0 (in Volts) is _____.




Answer: 0.5

Exp: For capacitor $Z_C = \frac{1}{j\omega C}$

Very high frequency means $\omega \rightarrow \infty \Rightarrow Z_C \rightarrow 0$

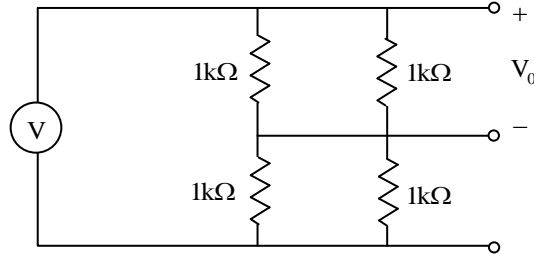So, all capacitors are replaced by short circuit.



By voltage division, $V_0 = \frac{V_i}{2}$

$$V_0 = \frac{1 \cdot \sin \omega t}{2} = 0.5 \sin \omega t$$

Thus, Peak voltage = 0.5

23. If the base width in a bipolar junction transistor is doubled, which one of the following statements will be TRUE?
- (A) Current gain will increase
 (B) Unity gain frequency will increase
 (C) Emitter base junction capacitance will increase
 (D) Early voltage will increase

Answer: (D)

Exp: W_B doubled (increased) \rightarrow early effect is still present but its effect less severe relative to previous W_B . Slope I_C Vs V_{CE} decreases

24. The value of $\sum_{n=0}^{\infty} n \left(\frac{1}{2}\right)^n$ is ____.

Answer: 2

Exp: Given that $\sum_{n=0}^{\infty} n \left(\frac{1}{2}\right)^n$


$$= 0 + 1 \cdot \frac{1}{2} + 2 \left(\frac{1}{2}\right)^2 + 3 \left(\frac{1}{2}\right)^3 + 4 \left(\frac{1}{2}\right)^4 + \dots$$

$$= \frac{1}{2} \left[1 + 2 \left(\frac{1}{2}\right) + 3 \left(\frac{1}{2}\right)^2 + 4 \left(\frac{1}{2}\right)^3 + \dots \right]$$

$$= \frac{1}{2} \left[1 - \frac{1}{2} \right]^{-2} \quad (\because (1-x)^{-2} = 1 + 2x + 3x^2 + 4x^3 + \dots)$$

$$= \frac{1}{2} \left(\frac{1}{2}\right)^{-2} = \left(\frac{1}{2}\right)^{-1} = 2$$

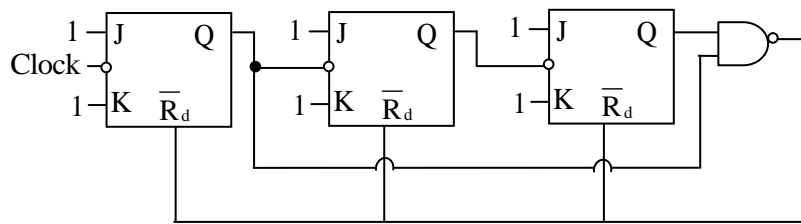25. The circuit shown consists of J-K flip-flops, each with an active low asynchronous reset ($\overline{R_d}$ input). The counter corresponding to this circuit is



- (A) a modulo-5 binary up counter (B) a modulo-6 binary down counter
(C) a modulo-5 binary down counter (D) a modulo-6 binary up counter

Answer: (A)

Exp: Analysis:


1. Clock is taken from normal output and it is -ve edge triggering. So, it is UP-counter.
2. Input of the NAND-gate is taken from Q_2 and Q_0 . So $Q_2 = 1$ and $Q_0 = 1$.
3. To find the modulus

$$(Q_2, Q_1, Q_0) = (1 \ 0 \ 1)$$

So, it is MOD - 5 binary UP-counter.


Q. No. 26 – 55 Carry Two Marks Each

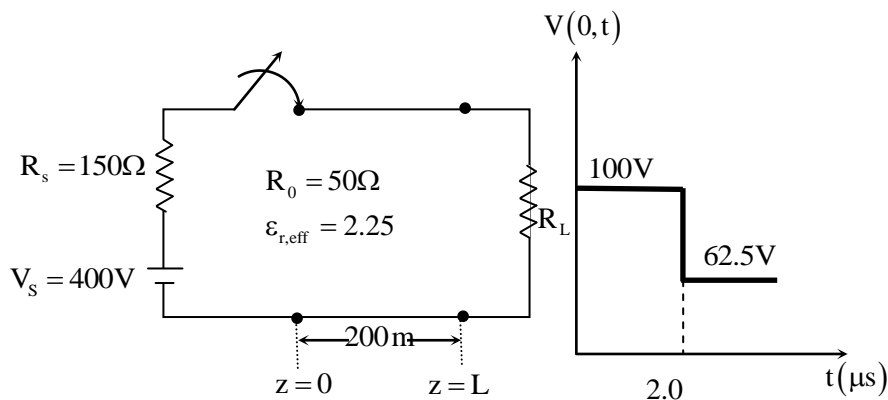26. A 200 m long transmission line having parameters shown in the figure is terminated into a load R_L . The line is connected to a 400 V source having source resistance R_s through a switch which is closed at $t = 0$. The transient response of the circuit at the input of the line ($z = 0$) is also drawn in the figure. The value of R_L (in Ω) is _____



Answer: 30

Exp:

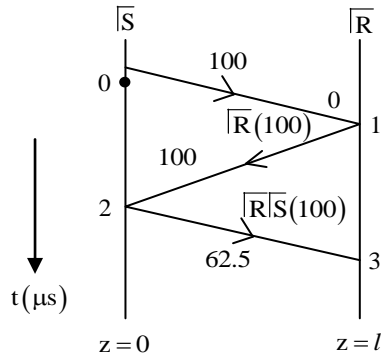

Given $V(t = 2\mu s, Z=0) = 62.5$

$$62.5 = V(t = 0, z = 0) + V(t = 1, z = 0) + V(t = 2, z = 0)$$

$$62.5 = 100 + \bar{R}(100) + \bar{R}\bar{S}(100)$$

$$\bar{R} = \frac{R_L - 50}{R_L + 50}, \bar{S} = \frac{1}{2}$$

$$\text{So, } \bar{R} = \frac{-1}{4},$$

$$R_L = 30\Omega$$

27. A coaxial capacitor of inner radius 1 mm and outer radius 5 mm has a capacitance per unit length of 172 pF/m. If the ratio of outer radius to inner is doubled, the capacitance per unit length (in pF/m) is _____.

Answer: 120.22

Exp: $C = \frac{2\pi \epsilon l}{\ln(b/a)}$

$$\frac{C}{l} = \frac{2\pi \epsilon}{\ln(b/a)} = C_1$$



$$\frac{C_1}{C_2} = \frac{\ln(b_2/a_2)}{\ln(b_1/a_1)}$$

$$\frac{172 \text{ pF}}{C_2} = \frac{\ln(10/1)}{\ln(5)}$$

$$C_2 = \frac{\ln(5)}{\ln(10)} 172 \text{ pF}$$

$$C_2 = 120.22 \text{ pF}$$

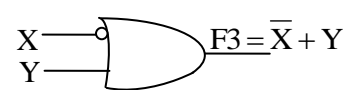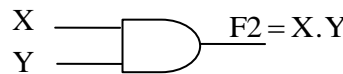28. A universal logic gate can implement any Boolean function by connecting sufficient number of them appropriately. Three gates are shown.



Which one of the following statements is TRUE?

- (A) Gate 1 is a universal gate.
- (B) Gate 2 is a universal gate.
- (C) Gate 3 is a universal gate.
- (D) None of the gates shown is a universal gate.

Answer: (C)

29. The Newton-Raphson method is used to solve the equation $f(x) = x^3 - 5x^2 + 6x - 8 = 0$. Taking the initial guess as $x = 5$, the solution obtained at the end of the first iteration is _____

Answer: 4.2903

Exp: $f(x) = x^3 - 5x^2 + 6x - 8$

$$x_0 = 5$$

$$f'(x) = 3x^2 - 10x + 6$$

By Newton-Raphson method.

$$x_1 = x_0 - \frac{f(x_0)}{f'(x_0)} = 5 - \frac{f(5)}{f'(5)}$$

$$= 5 - \frac{22}{31}$$

$$= 5 - 0.7097$$

$$= 4.2903$$



30. A random binary wave $y(t)$ is given by $y(t) = \sum_{n=-\infty}^{\infty} X_n p(t - nT - \phi)$.

where $p(t) = u(t) - u(t - T)$, $u(t)$ is the unit step function and ϕ is an independent random variable with uniform distribution in $[0, T]$. The sequence $\{X_n\}$ consists of independent and identically distributed binary valued random variables with $P\{X_n = +1\} = P\{X_n = -1\} = 0.5$ for each n .

The value of the auto correlation $R_{yy} \left(\frac{3T}{4} \right) \triangleq E \left[y(t)y \left(t - \frac{3T}{4} \right) \right]$ equals _____.

Answer: 0.25

Exp: $y(t) = \sum_{n=-\infty}^{\infty} X_n P(t - nT - \phi)$

$$R_{yy(\tau)} = \left[1 - \frac{|\tau|}{T} \right]$$


Derivation of above autocorrelation function can be found in any book dealing with random process.

[B.P. Lathi, Simon, Haykin, Schaum series].

$$R_{yy} \left(\frac{3T}{4} \right) = \left[1 - \frac{3\pi/4}{\pi} \right]$$

$$= \frac{1}{4} = 0.25$$

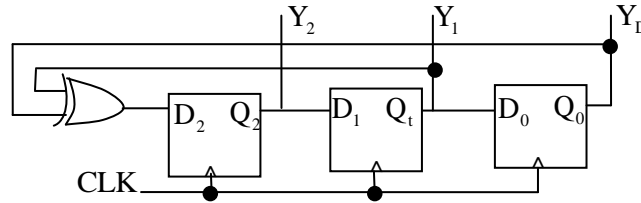31. A three bit pseudo random number generator is shown. Initially the value of output $Y = Y_2 Y_1 Y_0$ is set to 111. The value of output Y after three clock cycles is



- (A) 000 (B) 001
(C) 010 (D) 100


Answer: (D)

Exp:

	$D_2(Q_1 \oplus Q_0)$	$D_1(Q_2)$	$D_0(Q_1)$	$Y_2(Q_2)$	$Q_1(Y_1)$	$Q_0(Y_0)$
Initial	-	-	-	1	1	1
1 st clock	0	1	1	0	1	1
2 nd clock	0	0	1	0	0	1
3 rd clock	1	0	0	1	0	0


After three clock pulses output $Y_2 Y_1 Y_0 = 100$

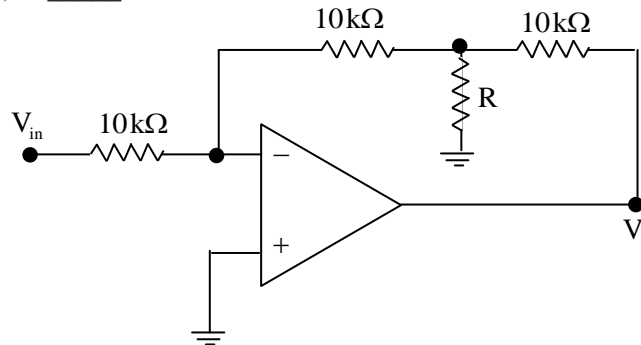32. In the circuit shown, assume that the opamp is ideal. If the gain (V_o/V_{in}) is -12, the value of R (in $k\Omega$) is _____



Answer: 1

Exp:

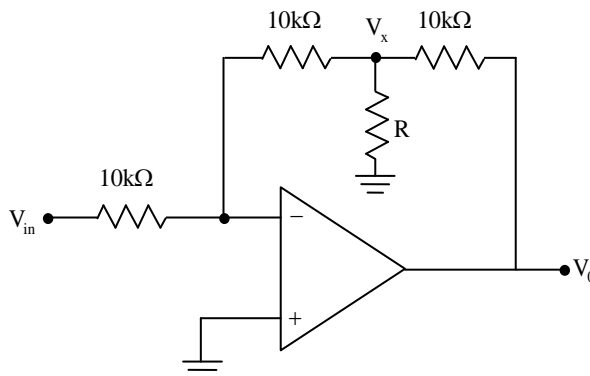

Apply nodal analysis at inverting terminal

$$\frac{V_{in} - 0}{10k} = \frac{0 - V_x}{10k} \Rightarrow V_{in} = -V_x \quad \text{--- (1)}$$

Again apply nodal analysis at node V_x

$$\frac{0 - V_x}{10k} = \frac{V_x - 0}{R} + \frac{V_x - V_0}{10k} \quad \text{--- (2)}$$

Put the value of V_x from equation (1) in equation (2) we get

$$R = 1k\Omega$$

33. Two sequences $x_1[n]$ and $x_2[n]$ have the same energy. Suppose $x_1[n] = \alpha 0.5^n u[n]$, where α is a positive real number and $u[n]$ is the unit step sequence. Assume

$$x_2[n] = \begin{cases} \sqrt{1.5} & \text{for } n = 0, 1 \\ 0 & \text{otherwise} \end{cases}$$

Then the value of α is _____.

Answer: 1.5

Exp: $x_1[n] = \alpha(0.5)^n u[n]$

$$\begin{aligned} \text{Energy of } x_1[n] &= \sum_{n=-\infty}^{\infty} x_1^2[n] \\ &= \sum_{n=0}^{\infty} \alpha^2 (0.5)^{2n} \end{aligned}$$

$$\begin{aligned} &= \alpha^2 \sum_{n=0}^{\infty} (0.25)^n \\ &= \alpha^2 \left[\frac{1}{1-0.25} \right] = \alpha^2 \left(\frac{4}{3} \right) \end{aligned}$$


$$\text{Energy of } x_2[n] = (\sqrt{1.5})^2 + (\sqrt{1.5})^2 = 3.$$

\therefore The energy of two sequences is same,

$$\alpha^2 \left(\frac{4}{3} \right) = 3 \Rightarrow \alpha^2 = \frac{9}{4}$$

$$\therefore \alpha = \frac{3}{2} = 1.5$$

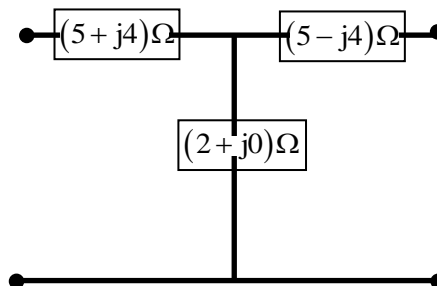34. The ABCD parameters of the following 2-port network are



$$(A) \begin{bmatrix} 3.5 + j2 & 20.5 \\ 20.5 & 3.5 - j2 \end{bmatrix}$$

$$(B) \begin{bmatrix} 3.5 + j2 & 0.5 \\ 0.5 & 3.5 - j2 \end{bmatrix}$$

$$(C) \begin{bmatrix} 10 & 2 + j0 \\ 2 + j0 & 10 \end{bmatrix}$$

$$(D) \begin{bmatrix} 7 + j4 & 0.5 \\ 30.5 & 7 - j4 \end{bmatrix}$$

Answer: (B)

Exp: For the standard 'T' network, obtain the Z-matrix first and then convert it into T-matrix

$$Z = \begin{bmatrix} 7 + j4 & 2 \\ 2 & 7 - j4 \end{bmatrix}$$

$$\Delta Z = [(7 + j4)(7 - j4)] - 4$$

$$= 49 + 16 - 4 = 61$$

$$A = \frac{Z_{11}}{Z_{21}} = \frac{7 + j4}{2} = 3.5 + j2$$

$$B = \frac{\Delta Z}{Z_{21}} = \frac{61}{2} = 30.5$$

$$C = \frac{1}{Z_{21}} = \frac{1}{2} = 0.5$$

$$D = \frac{Z_{22}}{Z_{21}} = \frac{7 - j4}{2} = 3.5 - j2$$

$$T = \begin{bmatrix} 3.5 + j2 & 30.5 \\ 0.5 & 3.5 - j2 \end{bmatrix}$$

35. A network is described by the state model as

$$\dot{x}_1 = 2x_1 - x_2 + 3u$$

$$\dot{x}_2 = -4x_2 - u$$

$$y = 3x_1 - 2x_2$$

The transfer function $H(s) \left(= \frac{Y(s)}{U(s)} \right)$ is

$$(A) \frac{11s + 35}{(s - 2)(s + 4)}$$

$$(B) \frac{11s - 35}{(s - 2)(s + 4)}$$

$$(C) \frac{11s + 38}{(s - 2)(s + 4)}$$

$$(D) \frac{11s - 38}{(s - 2)(s + 4)}$$

Answer: (A)


Exp: $A = \begin{bmatrix} 2 & -1 \\ 0 & -4 \end{bmatrix}$ $B = \begin{bmatrix} 3 \\ -1 \end{bmatrix}$

$$C = [3 \quad -2]$$

$$H(s) = C(sI - A)^{-1} B$$


$$\begin{aligned}
 &= [3 \quad -2] \begin{bmatrix} s-2 & 1 \\ 0 & s+4 \end{bmatrix}^{-1} \begin{bmatrix} 3 \\ -1 \end{bmatrix} \\
 &= [3 \quad -2] \frac{1}{(s-2)(s+4)} \begin{bmatrix} s+4 & -1 \\ 0 & s-2 \end{bmatrix} \begin{bmatrix} 3 \\ -1 \end{bmatrix} \\
 &= [3 \quad -2] \frac{1}{s^2+2s-8} \begin{bmatrix} 3s+12+1 \\ -s+2 \end{bmatrix} \\
 &= \frac{95+39+25-4}{(s-2)(s+4)} \\
 &= \frac{11s+35}{(s-2)(s+4)}
 \end{aligned}$$

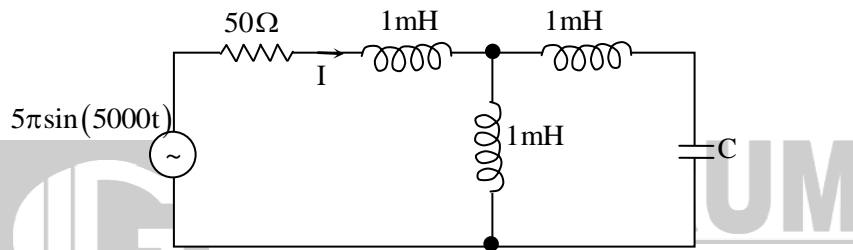36. In the circuit shown, the current I flowing through the 50Ω resistor will be zero if the value of capacitor C (in μF) is _____.



Answer: 20

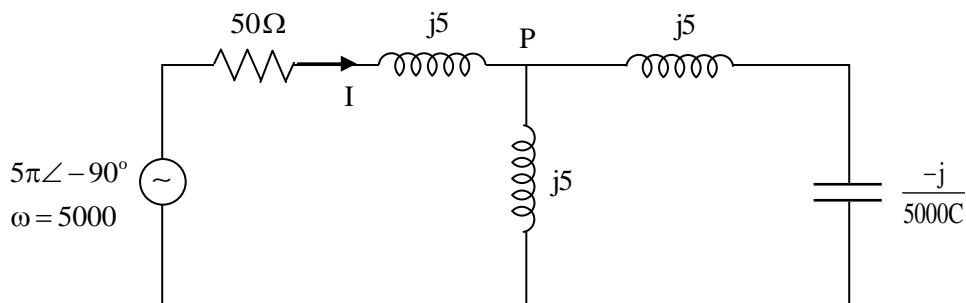Exp: Convert the network into phasor domain



If $I = 0$, $V_p = V_i$,

$$V_i \left(\frac{1}{j5} + \frac{1}{j \left(5 - \frac{1}{5000C} \right)} \right) = 0$$

$$\Rightarrow \frac{1}{j5} = -\frac{-1}{j \left(5 - \frac{1}{5000C} \right)} = 0$$


$$\frac{1}{5} = \frac{1}{\frac{1}{5000C} - 5}$$

$$\Rightarrow 5 = \frac{1}{5000C} - 5$$

$$\Rightarrow \frac{1}{5000C} = 10$$

$$\Rightarrow C = \frac{1}{5 \times 10^4} = 20 \mu\text{F}$$

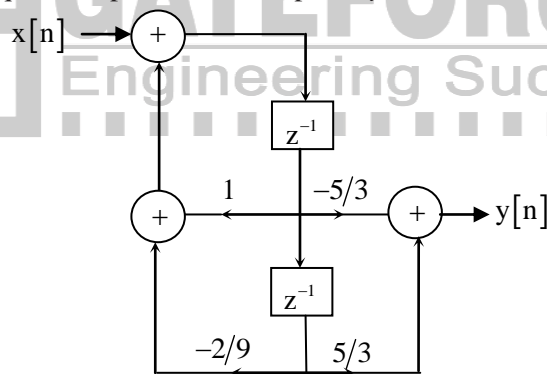37. A realization of a stable discrete time system is shown in figure. If the system is excited by a unit step sequence input $x[n]$, the response $y[n]$ is



(A) $4 \left(-\frac{1}{3} \right)^n u(n) - 5 \left(-\frac{2}{3} \right)^n u[n]$


(B) $5 \left(-\frac{2}{3} \right)^n u(n) - 3 \left(-\frac{1}{3} \right)^n u[n]$

(C) $5 \left(\frac{1}{3} \right)^n u(n) - 5 \left(\frac{2}{3} \right)^n u[n]$

(D) $5 \left(\frac{2}{3} \right)^n u(n) - 5 \left(\frac{1}{3} \right)^n u[n]$

Answer: (C)

Exp:

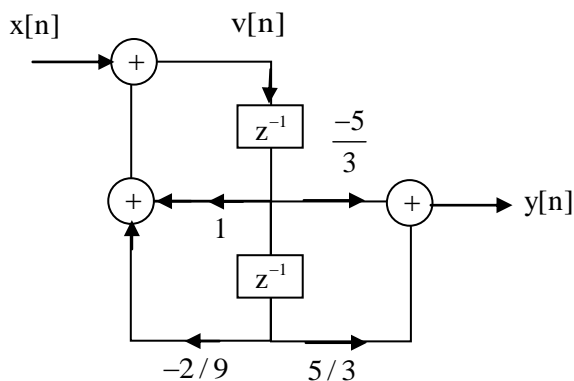

From the graph

$$v[n] = x[n] + v[n-1] - \frac{2}{9}v[n-2]$$

$$y[n] = -\frac{5}{3}v[n-1] + \frac{5}{3}v[n-2]$$

$$V(z) = \left[1 - z^{-1} + \frac{2}{9}z^{-2} \right] = X(z)$$

$$\Rightarrow \frac{V(z)}{X(z)} = \frac{1}{1 - z^{-1} + \frac{2}{9}z^{-2}} \rightarrow (1)$$

$$\frac{Y(z)}{V(z)} = \frac{-5}{3}z^{-1} + \frac{5}{3}z^{-2} \rightarrow (2)$$

Multiplying (1) and (2) we get

$$\Rightarrow \frac{Y(z)}{X(z)} = \frac{-\frac{5}{3}z^{-1}[1 - z^{-1}]}{1 - z^{-1} + \frac{2}{9}z^{-2}}$$

For unit step response, $X(z) = \frac{1}{1 - z^{-1}}$

$$\Rightarrow Y(z) = \frac{-\frac{5}{3}z^{-1}}{1 - z^{-1} + \frac{2}{9}z^{-2}}$$

$$= \frac{A}{1 - \frac{1}{3}z^{-1}} + \frac{B}{1 - \frac{2}{3}z^{-1}}$$

On solving,

$$A=5 ; B=-5$$

$$\Rightarrow y[n] = 5\left(\frac{1}{3}\right)^n u[n] - 5\left(\frac{2}{3}\right)^n u[n]$$

38. The complex envelope of the bandpass signal $x(t) = \sqrt{2} \left(\frac{\sin(\pi t/5)}{\pi t/5} \right) \sin\left(\pi t - \frac{\pi}{4}\right)$,

centered about $f = \frac{1}{2}$ Hz, is

- (A) $\left(\frac{\sin(\pi t/5)}{\pi t/5} \right) e^{j\frac{\pi}{4}}$ (B) $\left(\frac{\sin(\pi t/5)}{\pi t/5} \right) e^{-j\frac{\pi}{4}}$
- (C) $\sqrt{2} \left(\frac{\sin(\pi t/5)}{\pi t/5} \right) e^{j\frac{\pi}{4}}$ (D) $\sqrt{2} \left(\frac{\sin(\pi t/5)}{\pi t/5} \right) e^{j\frac{\pi}{4}}$

Answer: (C)

Exp: $x(t) = -\sqrt{2} \left(\frac{\sin(\pi t / 5)}{\pi t / 5} \right) \sin \left(\pi t - \frac{\pi}{4} \right)$

we can write above expression as

$$x(t) = -\sqrt{2} \left(\frac{\sin(\pi t / 5)}{\pi t / 5} \right) \left[\cos \frac{\pi}{4} \sin \pi t - \sin \frac{\pi}{4} \cos \pi t \right]$$

$$= \frac{\sin(\pi t / 5)}{\pi t / 5} \cos \pi t - \frac{\sin(\pi t / 5)}{(\pi t / 5)} \sin(\pi t)$$

Also

$$x(t) = x_c(t) \cos 2\pi f_c t - x_s(t) \sin(2\pi f_c t)$$

[Low pass representation of Bandpass signals]


$$x_c(t) = \frac{\sin(\pi t / 5)}{(\pi t / 5)}, x_s(t) = \frac{\sin(\pi t / 5)}{(\pi t / 5)}$$

$x_{ce}(t)$ is the complex envelope of $x(t)$

$$x_{ce}(t) = x_c(t) + jx_s(t)$$

$$= \frac{\sin(\pi t / 5)}{\pi t / 5} [1 + j] = \frac{\sqrt{2} \sin(\pi t / 5)}{(\pi t / 5)} e^{j\pi/4}$$

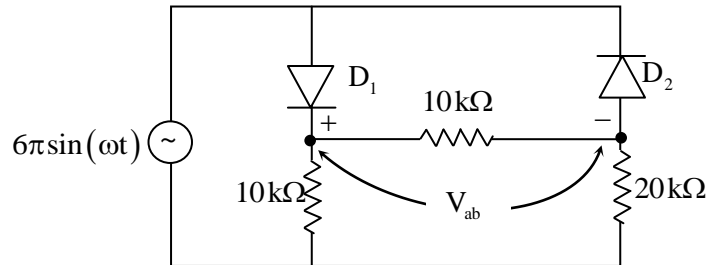39. In the circuit shown, assume that the diodes D_1 and D_2 are ideal. The average value of voltage V_{ab} (in Volts), across terminals 'a' and 'b' is _____.



Answer: 5

Exp: Input is positive half-cycle ($D_1 = \text{ON}, D_2 = \text{OFF}$)

$$V_{ab} = \frac{6\pi}{3} \sin \omega t = 2\pi \sin \omega t$$

Input is Negative half-cycle ($D_1 = \text{OFF}, D_2 = \text{ON}$)

$$V_{ab} = \frac{6\pi}{2} \sin \omega t = 3\pi \sin \omega t,$$

$$\text{Average of } V_{ab} = \frac{2\pi}{\pi} + \frac{3\pi}{\pi} = 5 \text{ volts}$$

40. Consider the differential equation

$$\frac{d^2x(t)}{dt^2} + 3\frac{dx(t)}{dt} + 2x(t) = 0.$$

Given $x(0) = 20$ and $x(1) = 10/e$, where $e = 2.71$. the value of $x(2)$ is _____

Answer: 0.8556

Exp: Given $\frac{d^2x(t)}{dt^2} + \frac{3dx(t)}{dt} + 2x(t) = 0$

$$x(0) = 20$$

$$x(1) = \frac{10}{e}$$

$$x(2) = \text{-----}$$

Auxillary equation is

$$m^2 + 3m + 2 = 0$$

$$m = -1, -2$$

Complementary solution $x_c = c_1e^{-t} + c_2e^{-2t}$

Particular solution $x_p = 0$

Finally $x = x_c + x_p = c_1e^{-t} + c_2e^{-2t}$

$$x(0) = 20 \Rightarrow 20 = c_1 + c_2 \rightarrow (a)$$

$$x(1) = \frac{10}{e} \Rightarrow \frac{10}{e} = c_1e^{-1} + c_2e^{-2}$$

$$\Rightarrow 10 = c_1 + c_2e^{-1} \rightarrow (b)$$

$$\text{From (a) } c_1 = 20 - c_2$$

$$\text{Now } 10 = (20 - c_2) + c_2e^{-1}$$

$$10 = c_2(e^{-1} - 1) + 20$$

$$c_2 = \frac{10 - 20}{e^{-1} - 1} = -\frac{10}{e^{-1} - 1} = \frac{10}{1 - e^{-1}} = \frac{10e}{e - 1}$$

$$\Rightarrow c_1 = 20 - \frac{10e}{e - 1} = \frac{20e - 20 - 10e}{e - 1} = \frac{10e - 20}{e - 1}$$

$$x(t) = \frac{10e - 20}{e - 1}e^{-t} + \frac{10e}{e - 1}e^{-2t}$$

$$x(2) = \left(\frac{10e - 20}{e - 1}\right)e^{-2} + \left(\frac{10e}{e - 1}\right)e^{-4} = 0.8556$$

41. Let $\tilde{x}[n] = 1 + \cos\left(\frac{\pi n}{8}\right)$ be periodic signal with period 16. Its DFS coefficient are defined

by $\alpha_k = \frac{1}{16} \sum_{x=0}^{15} \tilde{x}[n] \exp\left(-j\frac{\pi}{8}kn\right)$ for all k. The value of the coefficient α_{31} is _____.

Answer: 0.5

Exp: $x[n] = 1 + \cos\left(\frac{\pi}{8}n\right)$

$N=16$

$$x[n] = 1 + \frac{1}{2}e^{j\frac{2\pi n}{16}} + \frac{1}{2}e^{-j\frac{2\pi n}{16}}$$

$$a_{-1} = \frac{1}{2}, a_1 = \frac{1}{2}, a_0 = 1$$

$$a_1 = a_{-1+16} \Rightarrow a_{-1} = a_{15} = \frac{1}{2}$$

$$\Rightarrow a_0 = 1, a_1 = \frac{1}{2}, a_2 \text{ to } a_{14} = 0, a_{15} = \frac{1}{2}$$

DFS coefficients are also periodic with period 16.

$$a_{31} = a_{16+15}$$

$$a_{31} = a_{15}$$

$$\Rightarrow a_{31} = \frac{1}{2}$$

42. A fair die with faces $\{1, 2, 3, 4, 5, 6\}$ is thrown repeatedly till '3' is observed for the first time. Let X denote the number of times the die is thrown. The expected value of X is _____.

Answer: 6

Exp: Probability of getting 3 = $\frac{1}{6}$

$$\text{Probability of not getting 3} = 1 - \frac{1}{6} = \frac{5}{6}$$

If dice thrown repeatedly till first 3 observed first time then


$$E(x) = \frac{1}{6} + 2\left(\frac{5}{6} \times \frac{1}{6}\right) + 3\left(\frac{5}{6} \times \frac{5}{6} \times \frac{1}{6}\right) + \dots$$

$$= \frac{1}{6} \left[1 + 2\left(\frac{5}{6}\right) + 3\left(\frac{5}{6}\right)^2 + \dots \right]$$

$$= \frac{1}{6} \left[1 - \left(\frac{5}{6}\right) \right]^{-2}$$

$$= \frac{1}{6} \times 36 = 6$$

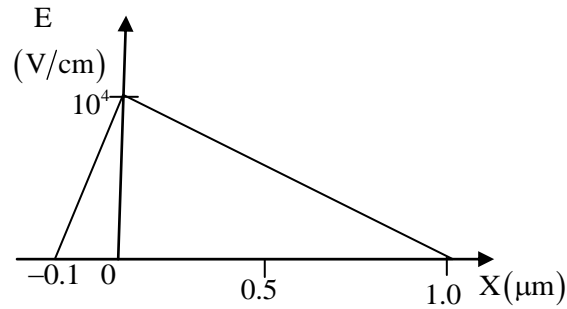43. The electric field profile in the depletion region of a $p-n$ junction in equilibrium is shown in the figure. Which one of the following statements is **NOT TRUE**?



- (A) The left side of the junction is n-type and the right side is p-type
 (B) Both the n-type and p-type depletion regions are uniformly doped
 (C) The potential difference across the depletion region is 700 mV
 (D) If the p-type region has a doping concentration of 10^{15} cm^{-3} , then the doping concentration in the n-type region will be 10^{16} cm^{-3}

Answer: (C)

Exp: Built in potential

$$\psi_0 = \frac{1}{2} \times \left(10^6 \frac{\text{V}}{\text{m}}\right) \times (1.1 \times 10^{-6} \text{ m})$$

$$= 0.55 \text{ volts}$$

But in Question (option C) is given as 700 mV.

44. A vector field $D = 2\rho^2 a_\rho + z a_z$ exists inside a cylindrical region enclosed by the surfaces $\rho = 1$, $z = 0$ and $z = 5$. Let S be the surface bounding this cylindrical region. The surface integral of this field on $S \left(\oint_S D \cdot ds \right)$ is _____.

Answer: 78.53

Exp: $D = 2\rho^2 a_\rho + z a_z$

$$\oint_S D \cdot ds = \int_V (\nabla \cdot D) dv$$

$$\nabla \cdot D = \frac{1}{\rho} \frac{\partial}{\partial \rho} (\rho D_\rho) + \frac{1}{\rho} \frac{\partial D_\phi}{\partial \phi} + \frac{\partial D_z}{\partial z}$$

$$= \frac{1}{\rho} \frac{\partial}{\partial \rho} (\rho 2\rho^2) + 0 + 1$$

$$= \frac{1}{\rho} 2(3)\rho^2 + 1$$

$$= 6\rho + 1$$

$$\int_V (\nabla \cdot D) dv = \int_{\rho=0}^1 \int_{\phi=0}^{2\pi} \int_{z=0}^5 (6\rho + 1) \rho \, d\rho d\phi dz$$

$$= \left(\frac{6\rho^3}{3} + \frac{\rho^2}{2} \right) \Big|_0^1 (2\pi)(5)$$

$$= \left(2 + \frac{1}{2} \right) 10\pi$$

$$\int_V (\nabla \cdot D) dv = 78.53$$

45. An npn BJT having reverse saturation current $I_s = 10^{-15}$ A is biased in the forward active region with $V_{BE} = 700$ mV. The thermal voltage (V_T) is 25 mV and the current gain (β) may vary from 50 to 150 due to manufacturing variations. The maximum emitter current (in μ A) is _____.

Answer: 1475

Exp: $I_B = \frac{I_C}{\beta} = \frac{I_S}{\beta} e^{V_{BE}/V_T}$


$$I_E = (\beta + 1) I_B$$

$$= \frac{\beta + 1}{\beta} I_S \cdot e^{V_{BE}/V_T}$$

$$= (1.02) (10^{-9} \times 10^{-6}) e^{\frac{700 \times 10^{-3}}{25 \times 10^{-3}}}$$

$$= 1475 \mu\text{A}$$

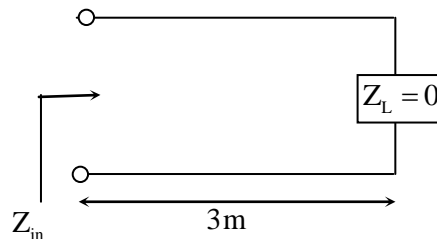46. Consider the 3 m long lossless air-filled transmission line shown in the figure. It has a characteristic impedance of $120\pi \Omega$, is terminated by a short circuit, and is excited with a frequency of 37.5 MHz. What is the nature of the input impedance (Z_{in})?



- (A) Open (B) Short (C) Inductive (D) Capacitive

Answer: (D)

Exp: $Z_{in} = jZ_0 \tan \beta l$

$$\beta l = \frac{2\pi}{\lambda} \cdot l \quad \left| \quad \lambda = \frac{3 \times 10^8}{37.5 \times 10^6} \right.$$

$$= \frac{2\pi}{8} (3) \quad \left| \quad = 8 \right.$$

$$= \frac{3\pi}{4}$$

Short circuited line

$$0 < \beta l < \frac{\pi}{2} \rightarrow \text{Inductor}$$

$$\frac{\pi}{2} < \beta l < \pi \rightarrow \text{Capacitor}$$

47. The current in an enhancement mode NMOS transistor biased in saturation mode was measured to be 1 mA at a drain-source voltage of 5 V. When the drain-source voltage was increased to 6 V while keeping gate-source voltage same, the drain current increased to 1.02 mA. Assume that drain to source saturation voltages is much smaller than the applied drain-source voltage. The channel length modulation parameter λ (in V^{-1}) is _____.

Answer: 0.022

Exp: NMOS SATURATION

$$I_D = 1\text{mA} @ V_{DS} = 5\text{V}$$

$$I_D = 1.02\text{mA} @ V_{DS} = 6\text{V}$$

$$V_{DSat} \ll V_{DS}$$

$$I_D = k (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

$$I_D = k'(1 + \lambda V_{DS})$$

$$10^{-3} = k'(1 + 5\lambda)$$


$$1.02 \times 10^{-3} = k'(1 + 6\lambda)$$

$$1.02 = \frac{1 + 6\lambda}{1 + 5\lambda} \Rightarrow 1.02 + 5.1\lambda = 1 + 6\lambda$$

$$0.02 = 0.9\lambda$$

$$\lambda = 0.022\text{V}^{-1}$$

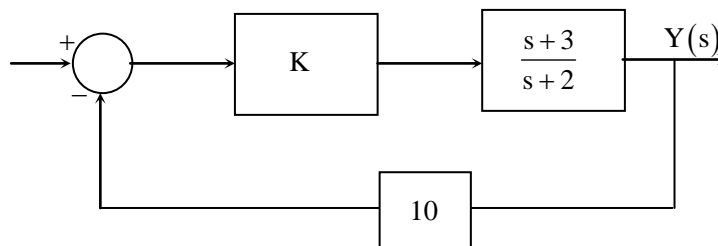48. For the system shown in figure, $s = -2.75$ lies on the root locus if K is _____.



Answer: 0.3


$$\begin{aligned} \text{Exp: } G(s)H(s) &= \frac{10k(s+3)}{(s+2)} \\ &= \frac{k'(s+3)}{(s+2)} \end{aligned}$$

For k'


$$k' = \frac{\text{Poles length}}{\text{zero length}} = \frac{0.75}{0.25} = 3$$

$$10k = 3$$

$$k = 0.3$$

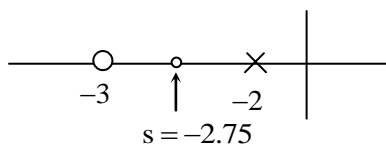

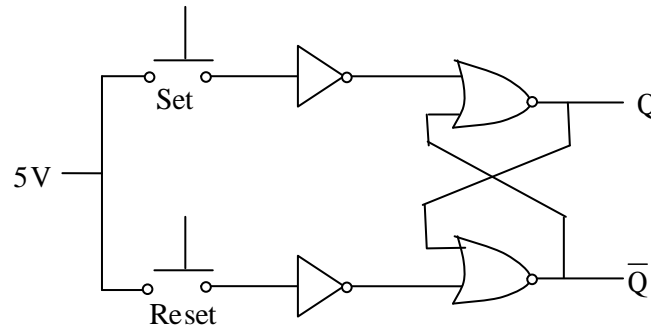49. An SR latch is implemented using TTL gates as shown in the figure. The set and reset pulse inputs are provided using the push-button switches. It is observed that the circuit fails to work as desired. The SR latch can be made functional by changing



- (A) NOR gates to NAND gates
(B) inverters to buffers
(C) NOR gates to NAND gates and inverters to buffers
(D) 5 V to ground

Answer: (D)

50. The variance of the random variable X with probability density function $f(x) = \frac{1}{2}|x|e^{-|x|}$ is _____

Answer: 6

Exp: Given that $f(x) = \frac{1}{2}|x|e^{-|x|}$ is probability density function of random variable X.

$$V(x) = E(x^2) - \{E(x)\}^2$$

$$E(x) = \int_{-\infty}^{\infty} xf(x) dx = \int_{-\infty}^{\infty} \frac{1}{2}|x|e^{-|x|} dx$$

$$= 0 \quad (\because \text{the function is odd})$$

$$E(x)^2 = \int_{-\infty}^{\infty} x^2 f(x) dx$$

$$= \int_{-\infty}^{\infty} x^2 \frac{1}{2}|x|e^{-|x|} dx$$

$$= \frac{2}{3} \int_0^{\infty} x^3 e^{-x} dx \quad (\because \text{function is even})$$

$$= 3! = 6$$

51. Consider a continuous-time signal defined as

$$x(t) = \left(\frac{\sin(at/2)}{(\pi t/2)} \right) * \sum_{n=-\infty}^{\infty} \delta(t-10n)$$

Where ‘*’ denotes the convolution operation and t is in seconds. The Nyquist sampling rate (in samples / sec) for x(t) is _____.

Answer: 0.4


$$\text{Exp: } x(t) = \frac{\sin(\pi t/2)}{(\pi t/2)} * \sum_{n=-\infty}^{\infty} \delta(t-10n)$$

Convolution in time domain becomes multiplication in frequency domain.


$$\frac{1}{10} \sum_{n=-\infty}^{\infty} \delta(f - kf_s)$$

$$F_s = \frac{1}{T_s} = 0.1$$


$$\frac{\sin(\pi t / 2)}{(\pi t / 2)}$$

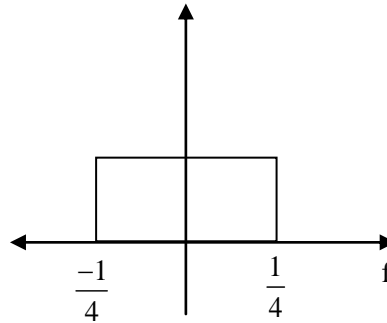
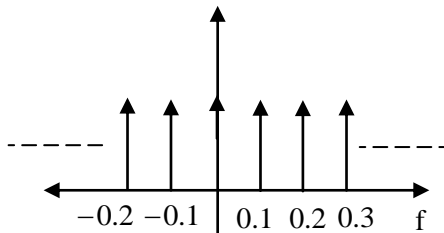
$$\sum_{n=-\infty}^{\infty} \delta(t - 10n)$$



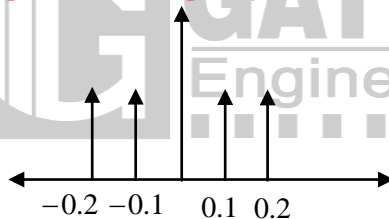Multiplication in frequency domain will result maximum frequency is 0.2.



Thus Nyquist rate = 0.4 samples/sec

52. In the circuit shown, the both the enhancement mode NMOS transistors have the following characteristics: $k_n = \mu_n C_{ox} (W/L) = 1 \text{ mA/V}^2$; $V_{TN} = 1\text{V}$. Assume that the channel length modulation parameter λ is zero and body is shorted to source. The minimum supply voltage V_{DD} (in volts) needed to ensure that transistor M_1 operates in saturation mode of operation is _____.

Answer: 3

Exp: Lower transistor (M_1) to work in saturation

$$V_{DS1} \geq V_{GS1} - V_+$$

So, for minimum V_{DD}

$$V_{DS1} = V_{GS1} - V_+$$

$$V_{DS1} = 2 - 1 = 1\text{V}$$


$$V_{DS1} = V_{D1} - V_{S1}$$

$$1\text{V} = V_{D1} - 0$$

$$\therefore V_{D1} = 1\text{V}$$

$$\text{and } I_{D1} = K'(V_{GS1} - V_+)^2$$
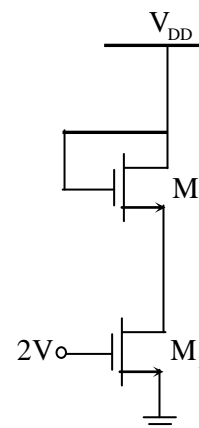
$$I_{D1} = \frac{1\text{mA}}{\text{V}^2} \times (2 - 1)^2 = 1\text{mA}$$



Now transistor M_2 , $V_{DG} = 0V$


So, it will work into saturation region and same current will flow

$$I_{D2} = I_{D1} = K'(V_{GS2} - V_+)^2$$

$$1mA = 1mA/V^2 \times (V_{DD} - 1 - 1)^2 \quad (\because V_{S2} = V_{D1})$$

$$\therefore V_{DD} = 3V$$

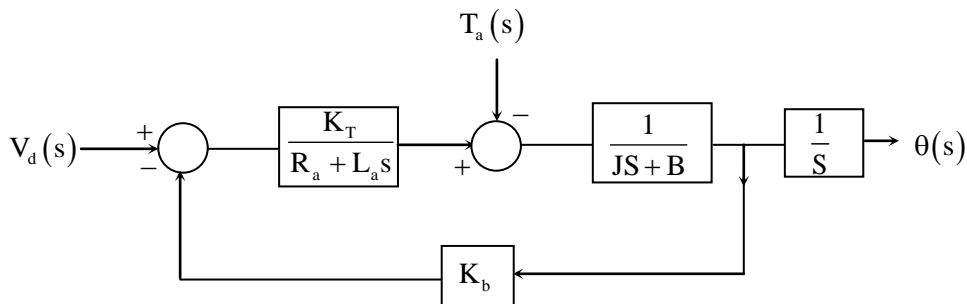53. The position control of a DC servo-motor is given in the figure. The values of the parameters are $K_T = 1 \text{ N-m/A}$, $R_a = 1 \Omega$, $L_a = 0.1H$, $J = 5 \text{ kg-m}^2$, $B = 1 \text{ N-m (rad/sec)}$ and $K_b = 1 \text{ V/(rad/sec)}$. The steady-state position response (in radians) due to unit impulse disturbance torque T_d is _____.



Answer: -0.5

Exp: $T_d(s) = 1$

$$\theta(s) = \frac{1}{s \left[(Js + B) + \frac{K_b K_T}{R_a + L_a s} \right]}$$

Steady State Value is $\lim_{s \rightarrow 0} s\theta(s) = -0.5$

54. The characteristic equation of an LTI system is given by $F(s) = s^5 + 2s^4 + 3s^3 + 6s^2 - 4s - 8 = 0$. The number of roots that lie strictly in the left half s-plane is _____.

Answer: 2

Exp: $s^5 + 2s^4 + 3s^3 + 6s^2 - 4s - 8 = 0$

S^5	1	3	-4	
S^4	2	6	-8	
S^3	8	12	0	
S^2	3	-8	0	$\rightarrow as \in \rightarrow 0$
S^1	-9.33	0	0	
S^0	-8			

$$2s^4 + 6s^2 - 8 = 0$$

Let $x = s^2$, then

$$2x^2 + 6x - 8 \Rightarrow x = 1, -4$$

$$s^2 = 1, -4 \Rightarrow s = \pm 1, \pm 2j$$

Number of roots lies on RHS $\rightarrow s = 1$


There are only two poles left on LHS.

55. Suppose $x[n]$ is an absolutely summable discrete-time signal. Its z -transform is a rational function with two poles and two zeroes. The poles are at $z = \pm 2j$. Which one of the following statements is TRUE for the signal $x[n]$?

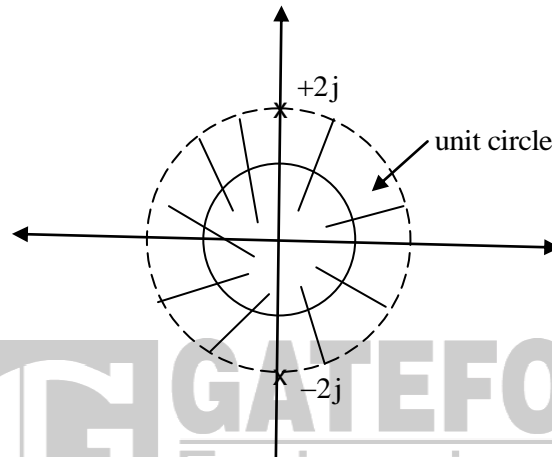- (A) It is a finite duration signal. (B) It is a causal signal.
(C) It is a non-causal signal. (D) It is a periodic signal

Answer: (C)

Exp: Since $x[n]$ is absolutely summable thus its ROC must include unit circle.



Thus ROC must be inside the circling radius 2.

$x[n]$ must be a non-causal signal.